

TEST BOARD LCR EVALUATION

(FOR DC-DC CONVERTER)

VINCE WEI

04/20/2016


TOPICS

- **Parasitic parameters of PCB trace**
- **LCR analysis**
- **Transmission line**

FEATURE OF TEST BOARD (DC-DC)

- Long traces (test head dimension and cable)
- Wide traces (high current)
- Additional components (relays, buffers, servo-loop etc.)
- Multi-traces (multi-resources per pin)
- Multi-sites (parallel test)
- Multi-layers (noise isolation)

PARASITIC MODEL

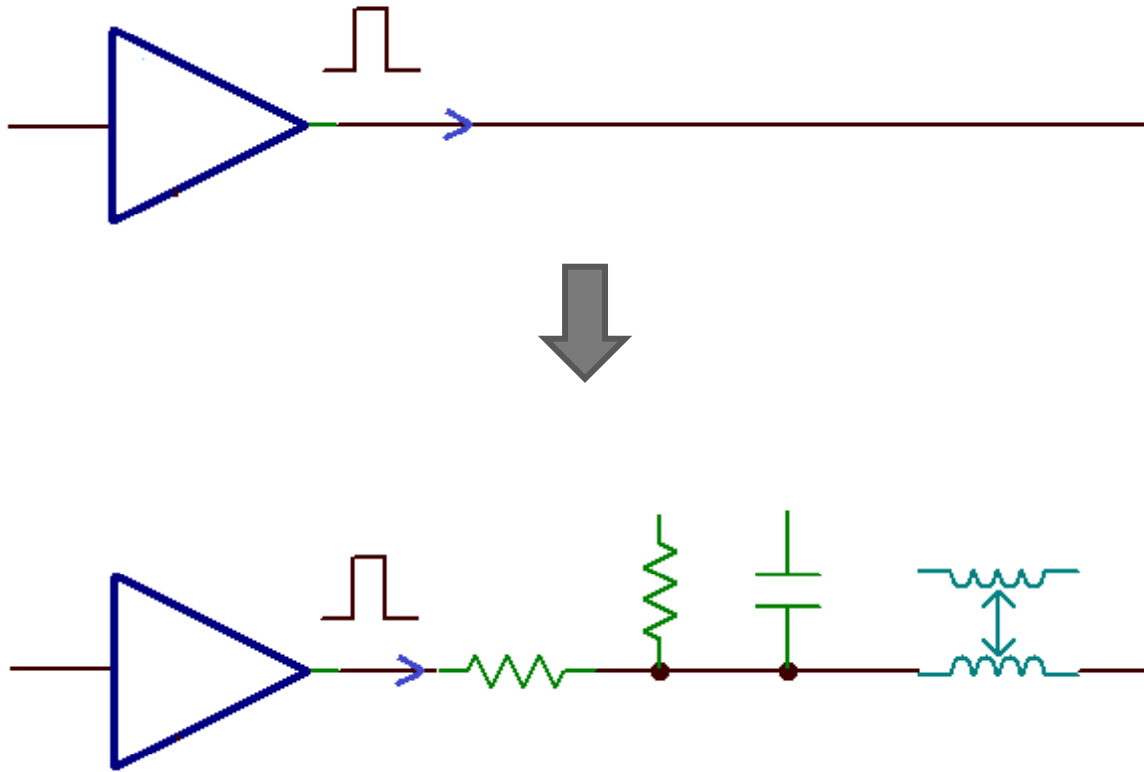

MODEL OF PCB TRACE


W: Width of trace

T: Thickness of trace


H: Distance of trace and copper plate

Er: Dielectric constant


Tool: Saturn PCB Toolkit

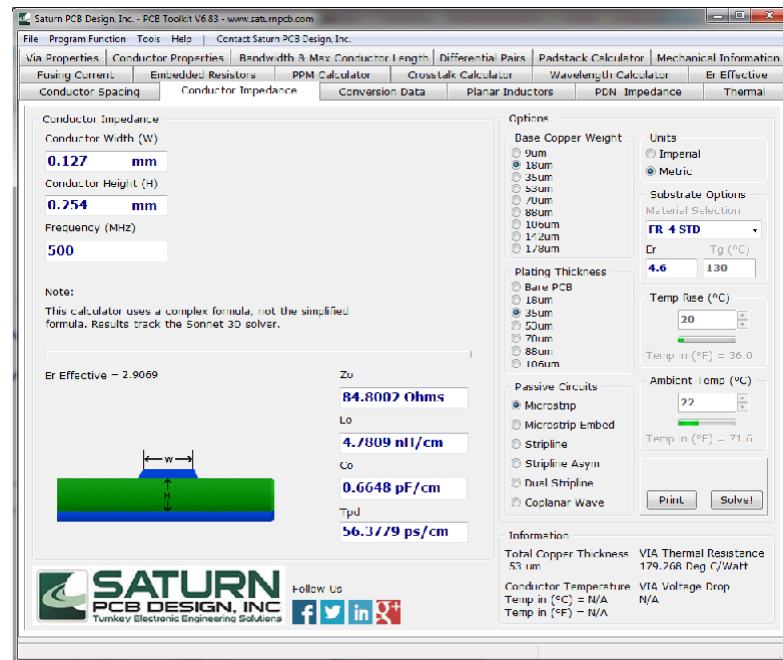


Micro-Strip

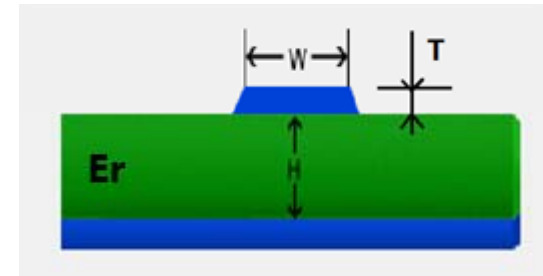

Micro-Strip Embed

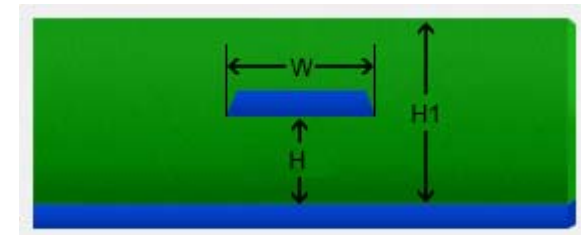

Strip-Line

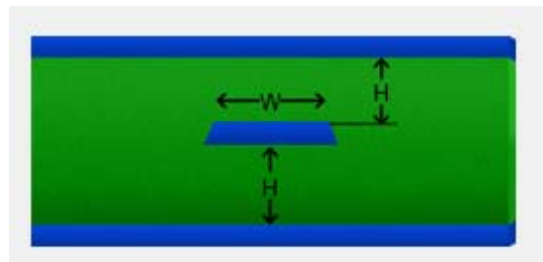


COMPARISON

T=35um (1OZ)

ER=4.6 (FR-4)

W=0.127mm

H=0.127mm

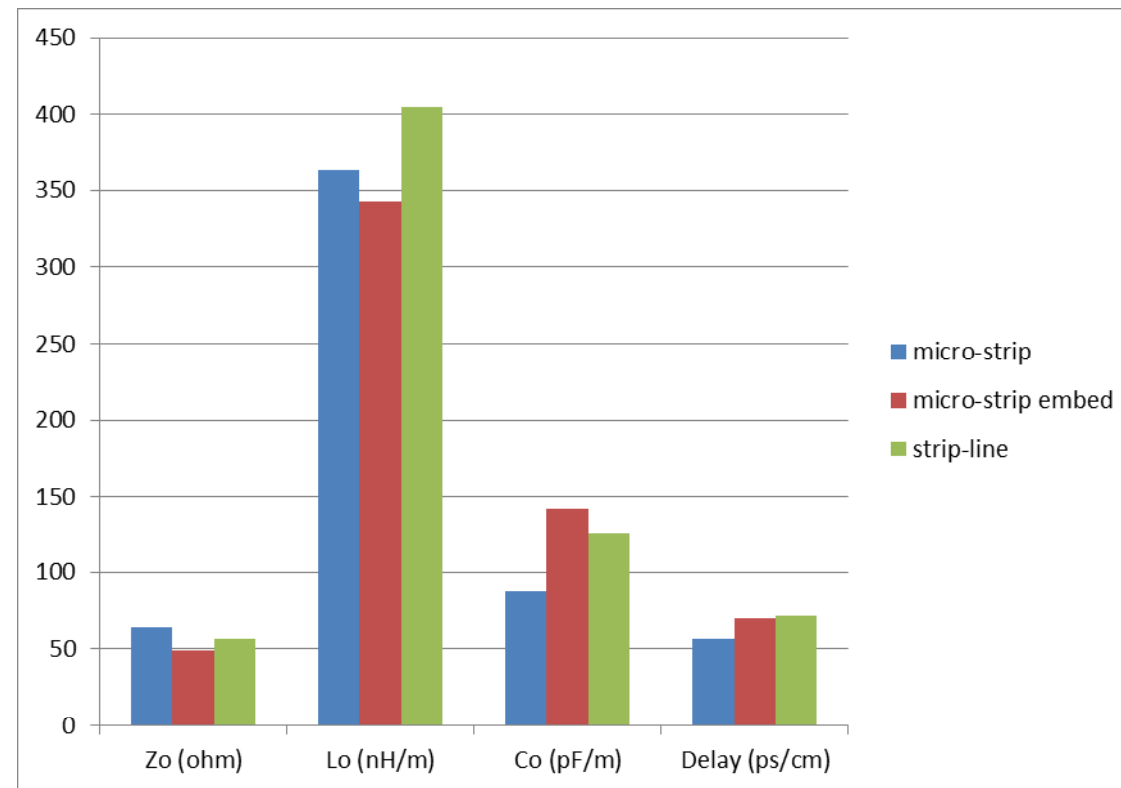


TRACE CAPACITANCE

T=35um (10Z)

ER=4.6 (FR-4)

$Ea=8.86 \cdot 10^{-12} \text{F/m}$

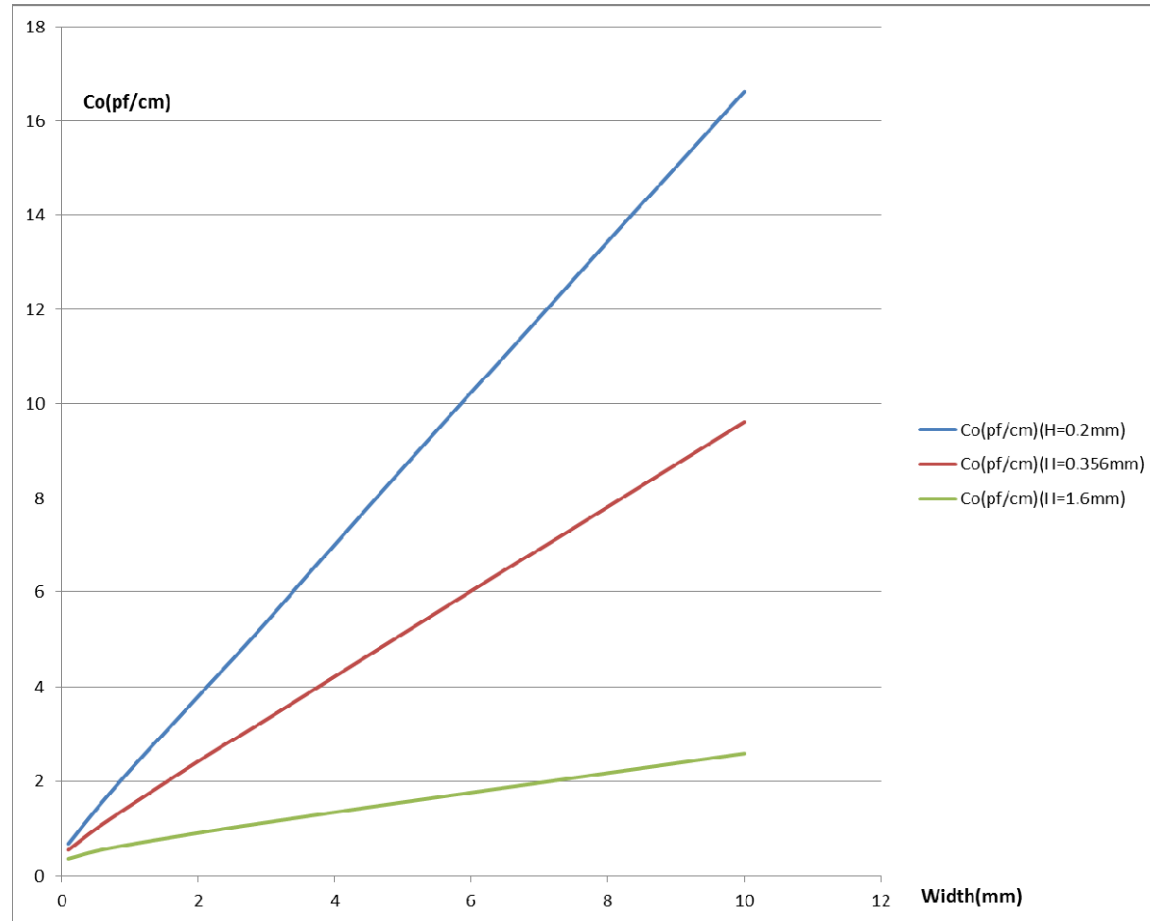$C=W \cdot l \cdot Ea \cdot Er / H \text{ (F)}$




TRACE INDUCTANCE

T=35 μm (1OZ)

ER=4.6 (FR-4)
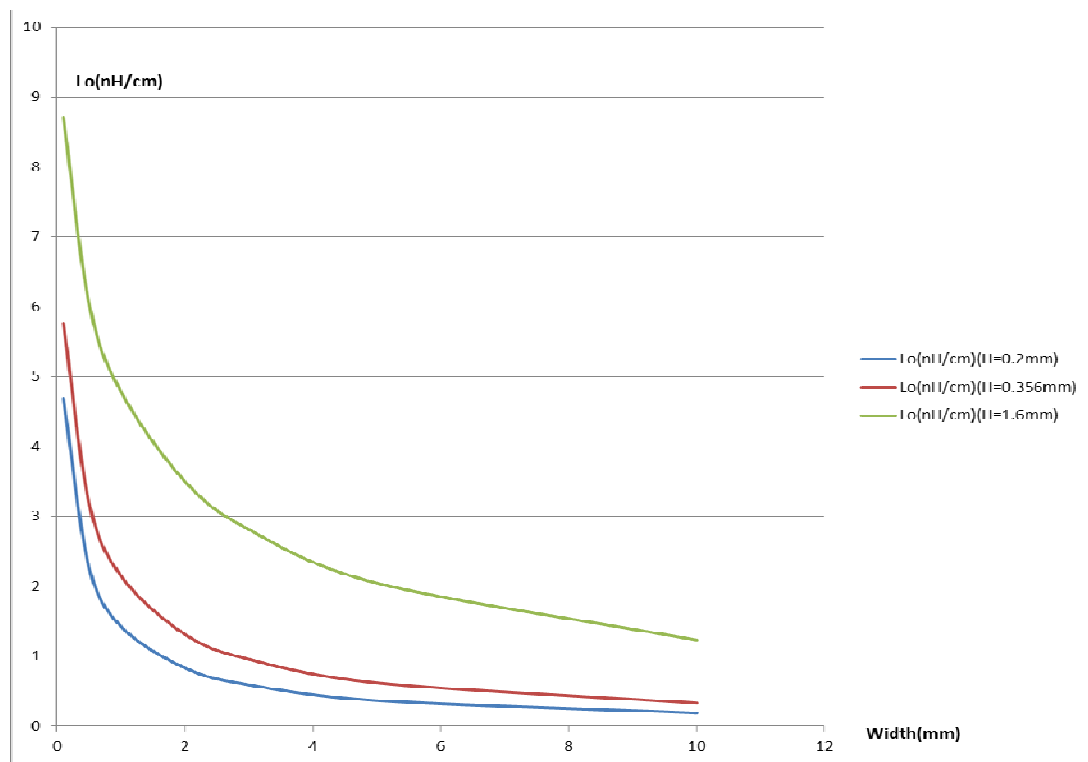
$$L = 200 * l * (\ln(2l/(W+T)) + 0.5 + 0.2235(W+T)/l) \text{ (nH)}$$




TRACE RESISTANCE

T=35um (10Z)

ER=4.6 (FR-4)

$\rho_{Cu}=1.75 \times 10^{-8} \Omega \cdot m$

$R = \rho L / S \ (\Omega)$

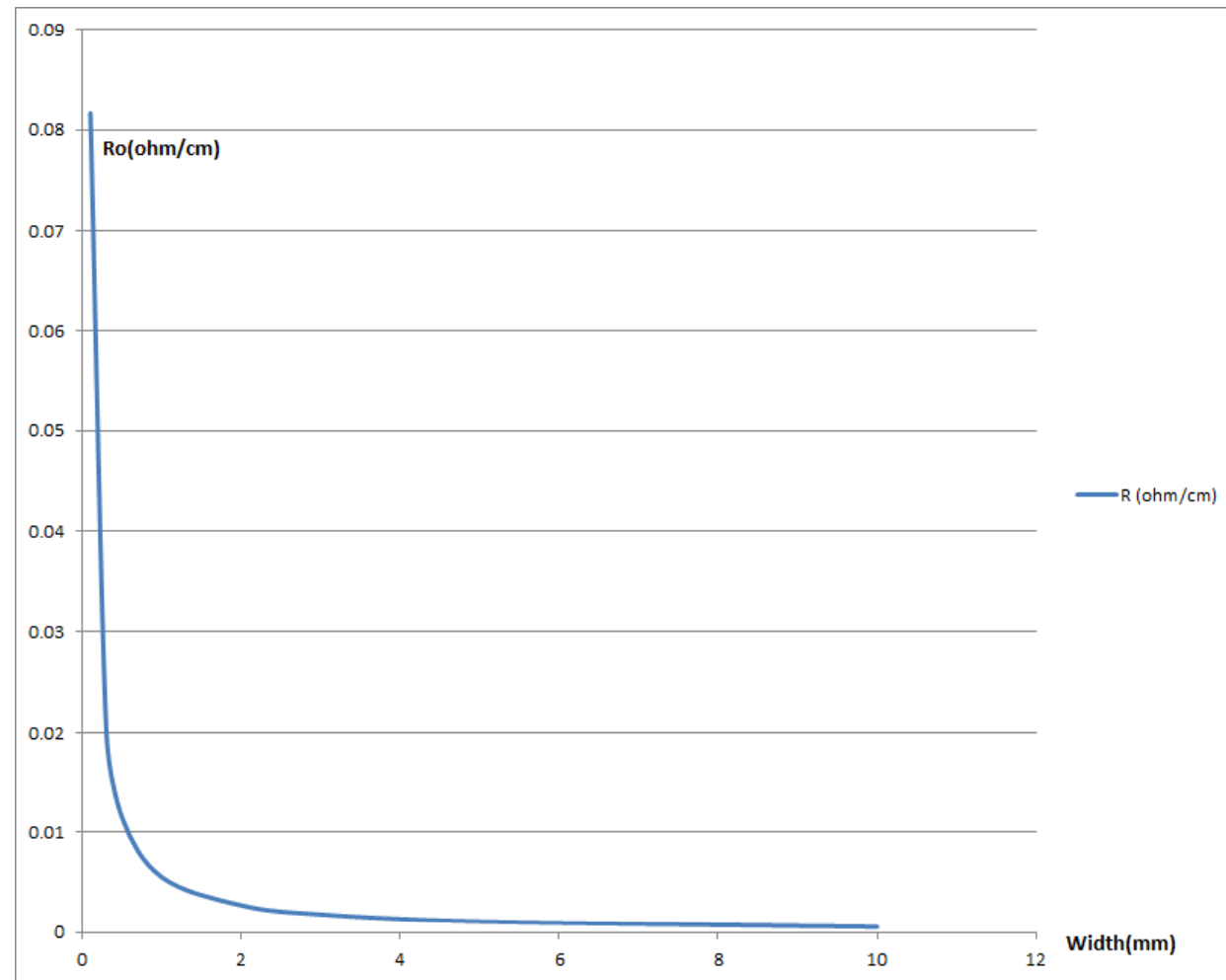


SINE WAVE RESPONSE


$$X_R = R$$

$$X_C = 1/(2 \pi f C)$$


$$X_L = 2 \pi f L$$

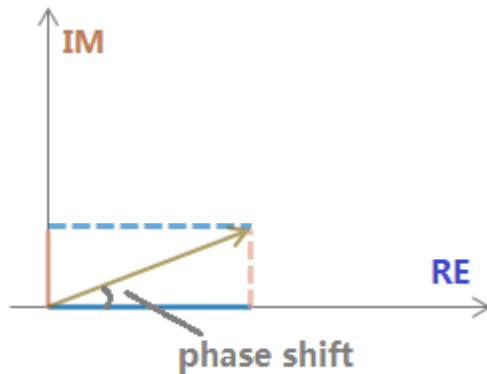

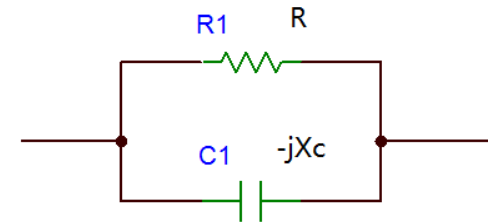
$$Z = \frac{-jXR}{(R - jX)} = (RX^2 - jXR^2)/(R^2 + X^2)$$


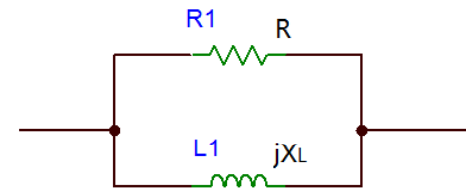
$$Z = \frac{jXR}{(R + jX)} = (RX^2 + jXR^2)/(R^2 + X^2)$$



$$Z = R + jX_L - jX_C$$

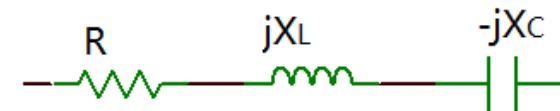

LCR ZERO-INPUT RESPONSE

$$R^2 C - 4 L > 0:$$



$$u_c = u_{c0} \left[\left(\frac{L i_0}{C k U_{c0}} + \frac{R}{2k} + \frac{1}{2} \right) e^{\frac{k-R}{2L} t} - \left(\frac{L i_0}{C k U_{c0}} + \frac{R}{2k} - \frac{1}{2} \right) e^{-\frac{k+R}{2L} t} \right]$$

$$= u_{c0} \left[\left(\frac{L i_0}{C k U_{c0}} + \frac{R}{2k} + \frac{1}{2} \right) e^{\frac{-2}{CR+CK} t} - \left(\frac{L i_0}{C k U_{c0}} + \frac{R}{2k} - \frac{1}{2} \right) e^{\frac{-2}{CR-CK} t} \right]$$

$$i_c = i_0 \left[\left(\frac{-R}{2k} + \frac{1}{2} - \frac{U_0}{k i_0} \right) e^{\frac{k-R}{2L} t} - \left(\frac{-R}{2k} - \frac{1}{2} - \frac{U_0}{k i_0} \right) e^{-\frac{k+R}{2L} t} \right]$$

$$\beta = \sqrt{\frac{R^2 C - 4 L}{4 C L^2}} = \frac{k}{2L} \quad (k = \sqrt{R^2 - 4 L / C})$$
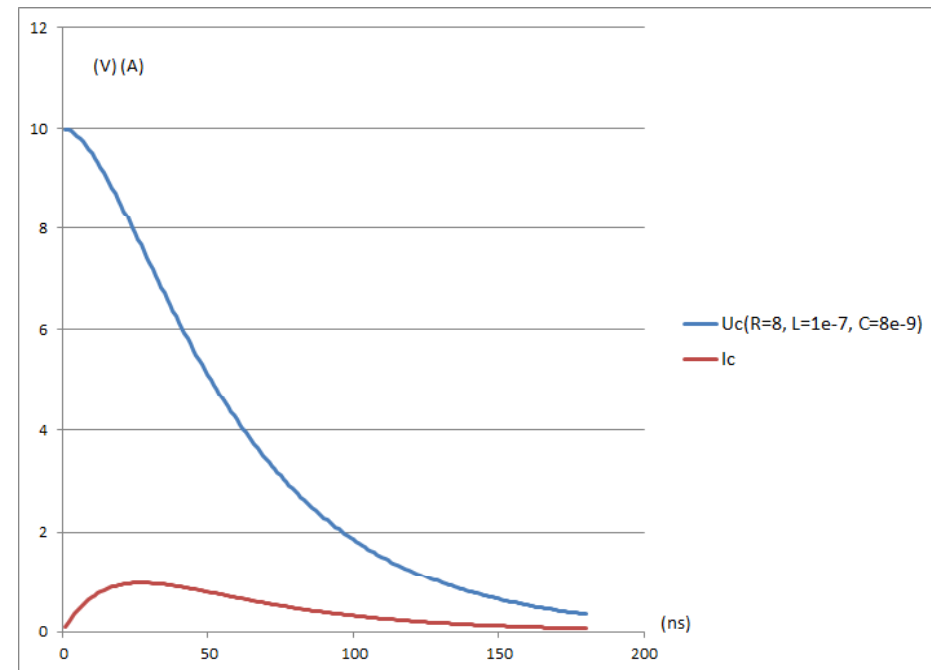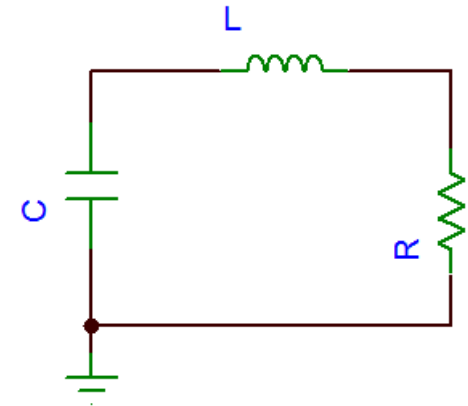
$$\tau_1 = \frac{CR+CK}{2} \quad \left(\frac{CR}{2} < \tau < CR \right)$$



LCR ZERO-INPUT RESPONSE

$$R^2 C - 4 L < 0:$$



$$u_c = u_{c0} e^{(-\frac{1}{\tau} t)} \left[\left(\frac{2L i_0}{m C u_{c0}} + \frac{R}{m} \right) \sin(\omega t) + \cos(\omega t) \right]$$

$$i_c = -i_0 e^{(-\frac{1}{\tau} t)} \left[\left(\frac{R i_0 + 2u_{c0}}{m i_0} \right) \sin(\omega t) - \cos(\omega t) \right]$$

$$\omega = \sqrt{\frac{4 L - R^2 C}{4 C L^2}} = \frac{m}{2L}$$

$$(m = \sqrt{-R^2 + 4 L / C})$$

$$\tau = \frac{2 L}{R}$$

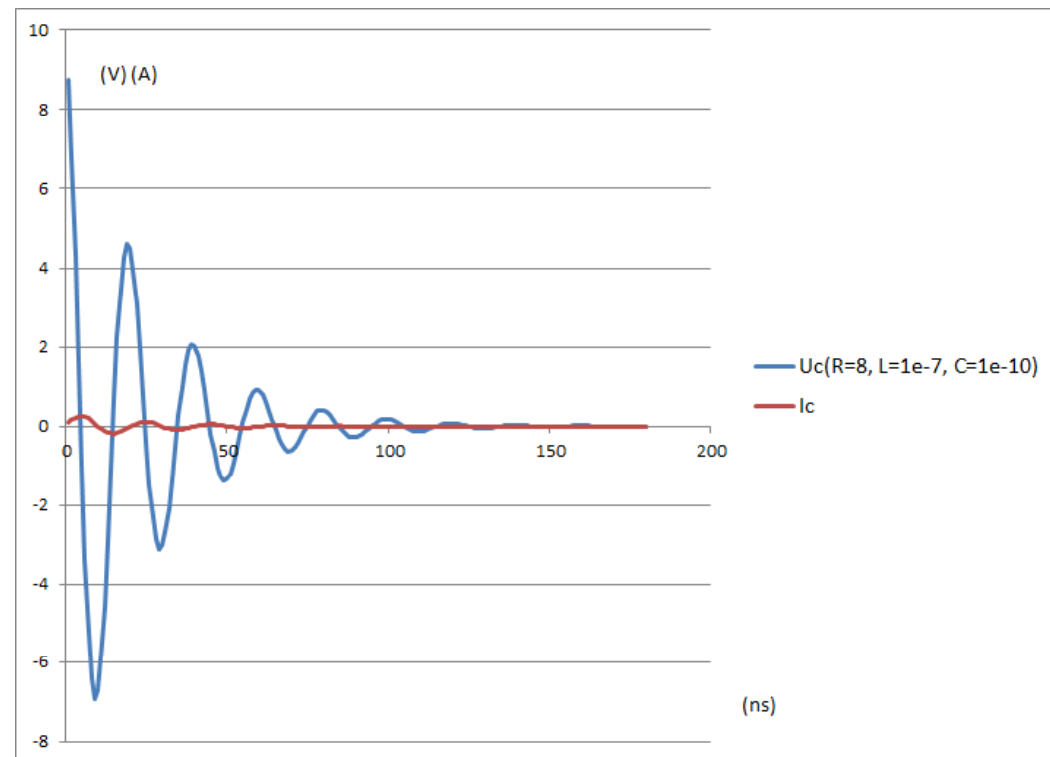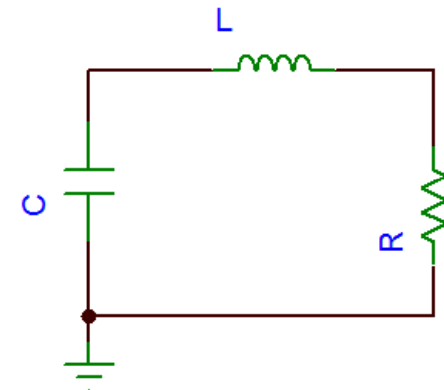



LCR ZERO-INPUT RESPONSE

$$R^2 C - 4 L = 0:$$


$$u_c = u_{c0} e^{(-\frac{1}{\tau}t)} \left[\left(\frac{i_0}{C u_{c0}} + \frac{R}{2L} \right) t + 1 \right]$$

$$i_c = i_0 e^{(-\frac{1}{\tau}t)} \left\{ \left(-\frac{R}{2L} - \frac{u_{c0}}{L i_0} \right) t + 1 \right\}$$

$$\tau = \frac{2L}{R} = \frac{RC}{2}$$

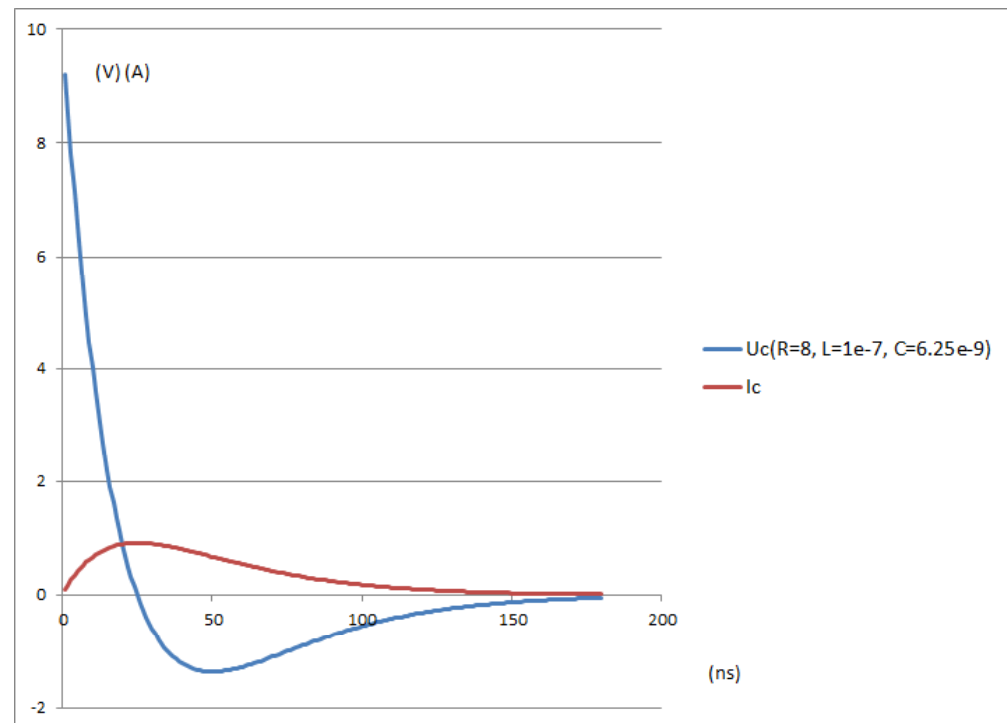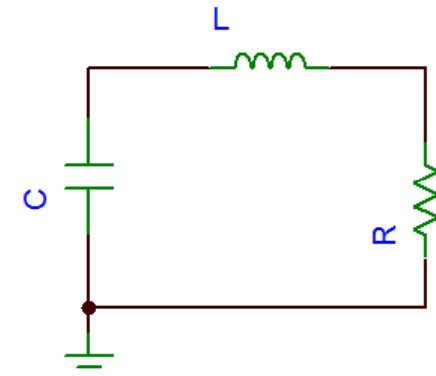

TIME CONSTANT "T"

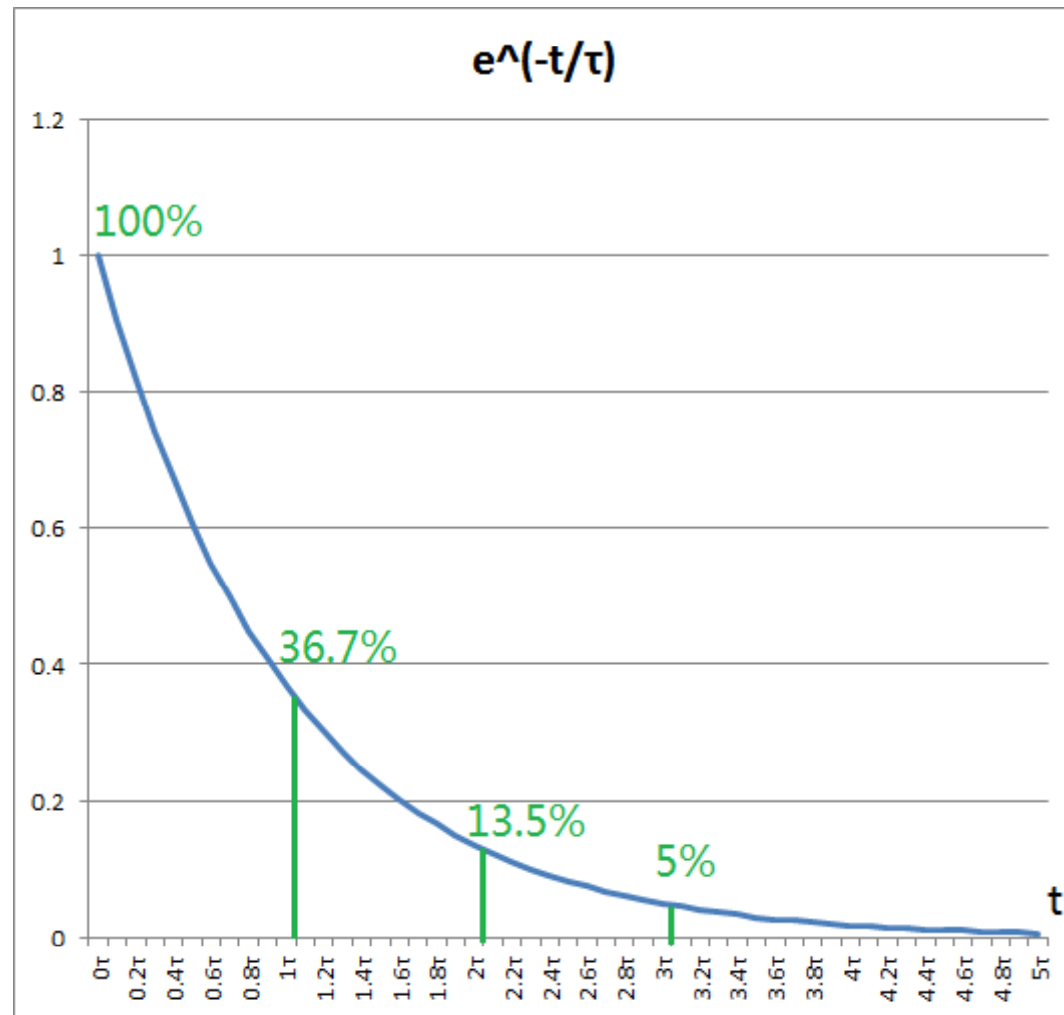


LCR SPECIAL CASE ($R^2 \ll 4 L/C$)

1) $R^2 \ll \frac{4L}{C}$

$$u_c = u_{c0} \left[\left(\frac{i_0}{\omega C u_{c0}} \right) \sin(\omega t) + \cos(\omega t) \right]$$

$$\omega = \sqrt{\frac{4L - R^2 C}{4CL^2}} = \sqrt{\frac{1}{CL}}$$

$$\tau = \frac{2L}{R} = \infty$$

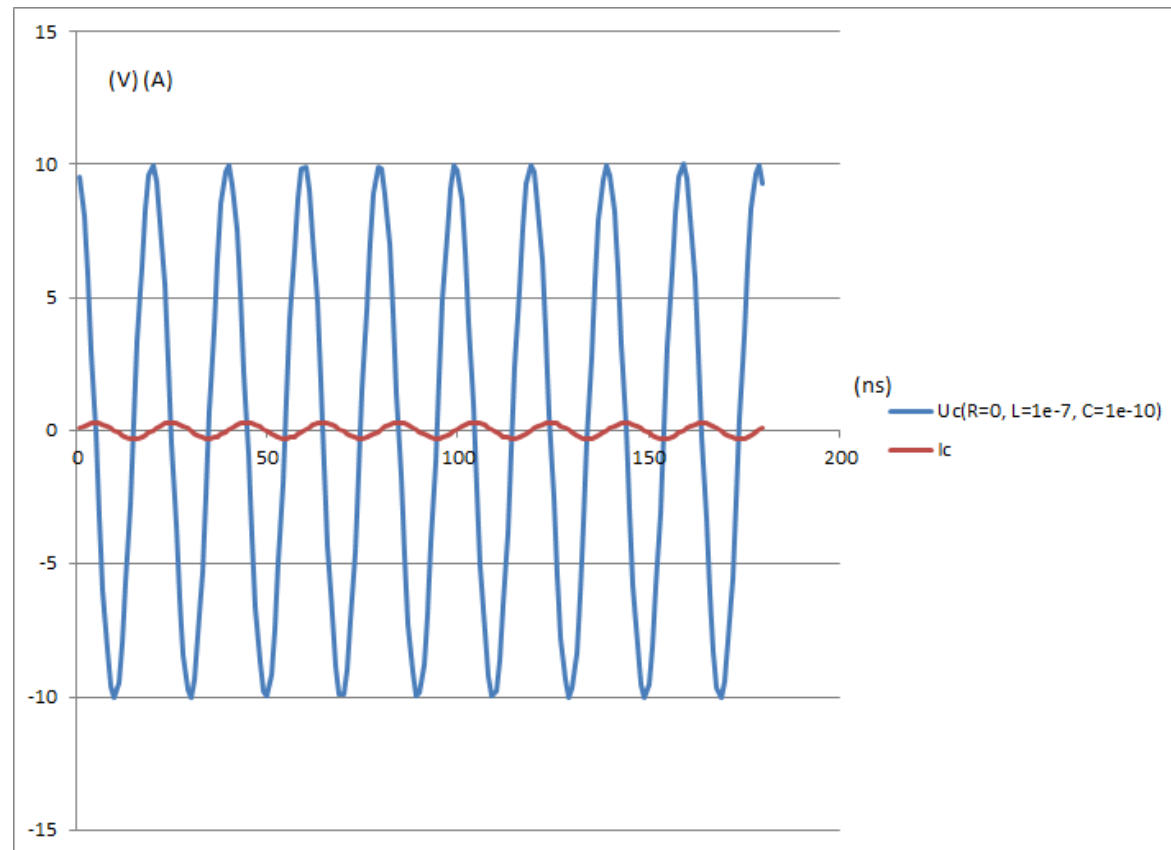


LCR SPECIAL CASE($C \gg R^2/(4 L)$)

2) $C \gg R^2/(4 L)$

$$u_R = -i_C R$$
$$= U_0 - (Ri_0 + U_0)e^{-\frac{R}{L}t}$$

$$\tau_1 = \frac{L}{R}$$

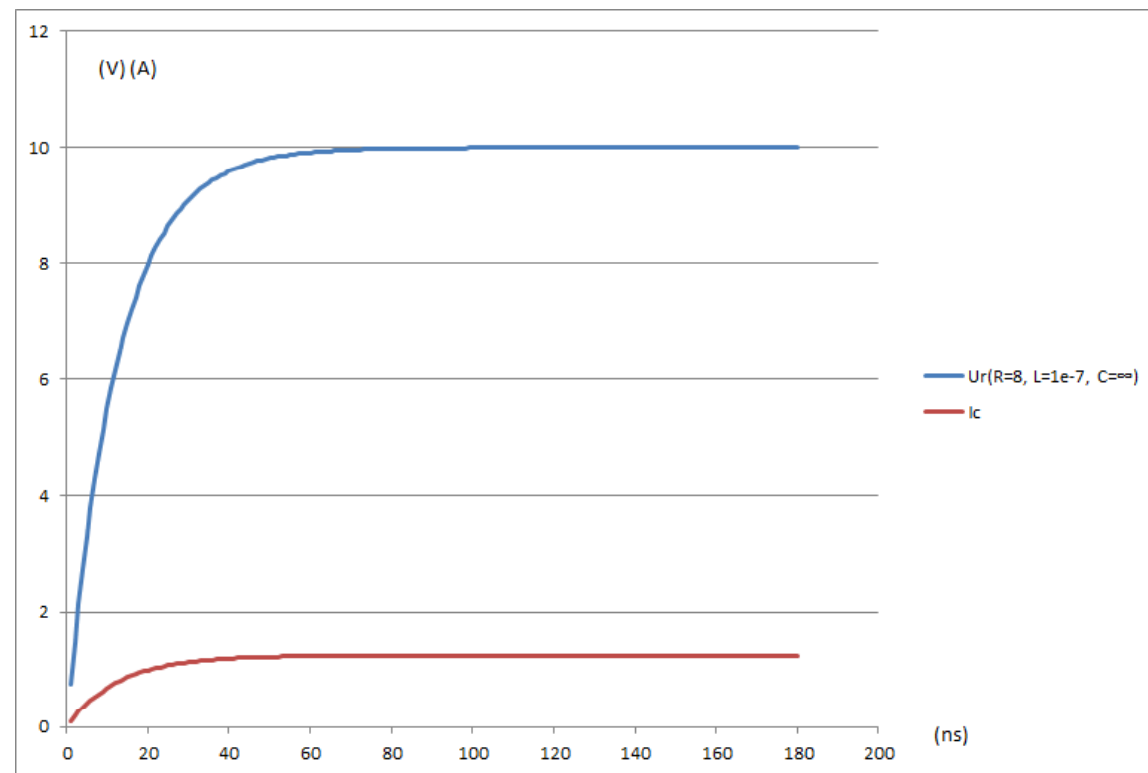


LCR SPECIAL CASE($L \ll R^2C/4$)

3) $L \ll R^2C/4$

$$u_c = u_{c0} e^{-\frac{1}{RC}t}$$

$$\tau_1 = RC$$

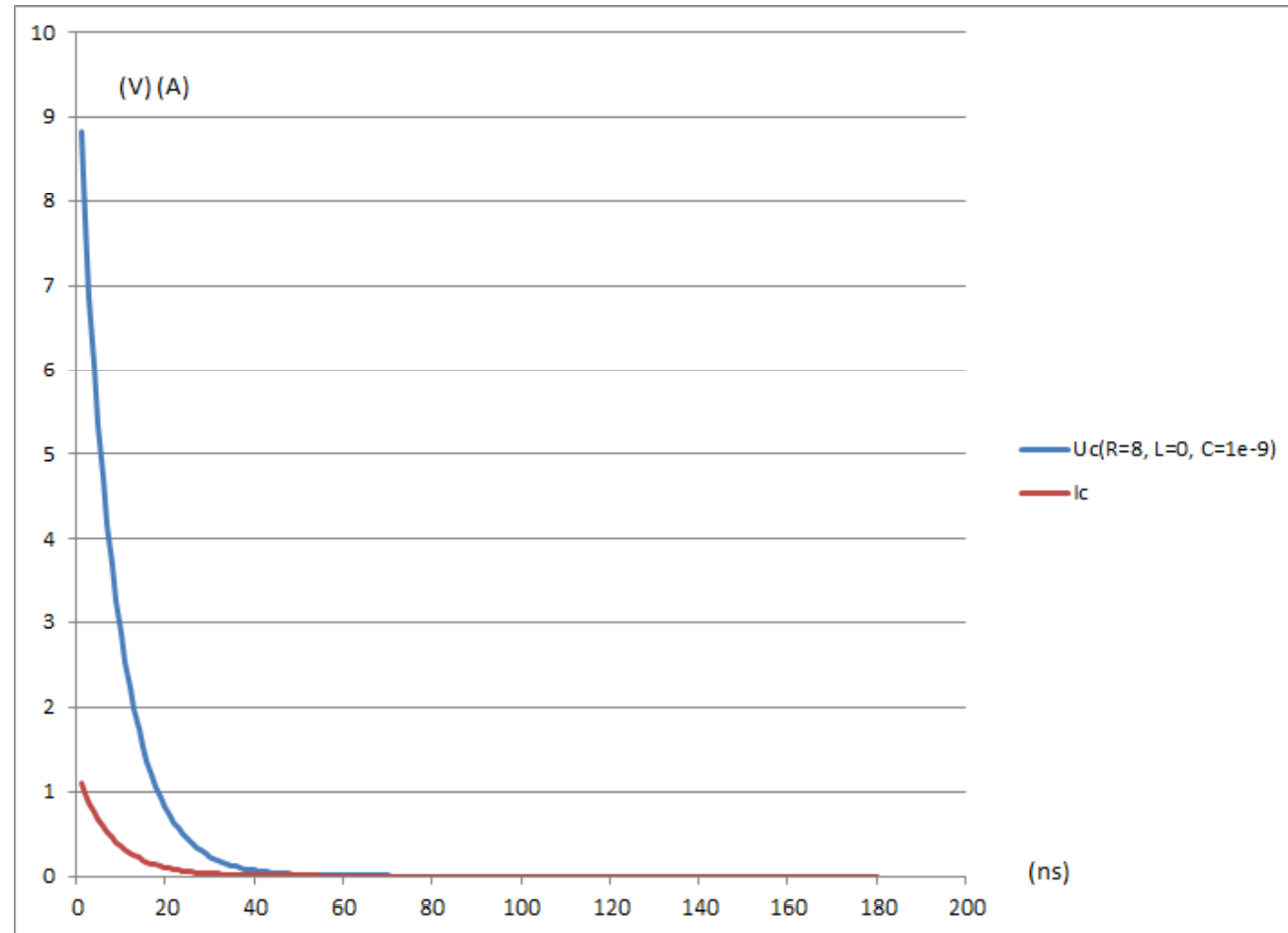



CIRCUIT1

$L1=40\text{nH}$
 $R1=10\text{Kohm}$
 $R2=100\text{ohm}$
 $L2=40\text{nH}$
 $C1=200\text{pF}$

1) FET on
 $L_2 \ll R_2^2 C_1 / 4$
 $\tau_{fal} = R_2 C_1 = 20\text{e-}9$

2) FET off
 $L_1 + L_2 < R_1^2 C_1 / 4$
 $\tau_{ris} = R_1 C_1 = 2\text{e-}6$

Solution:
 Smaller R1?
 Narrower trace?
 Buffer?

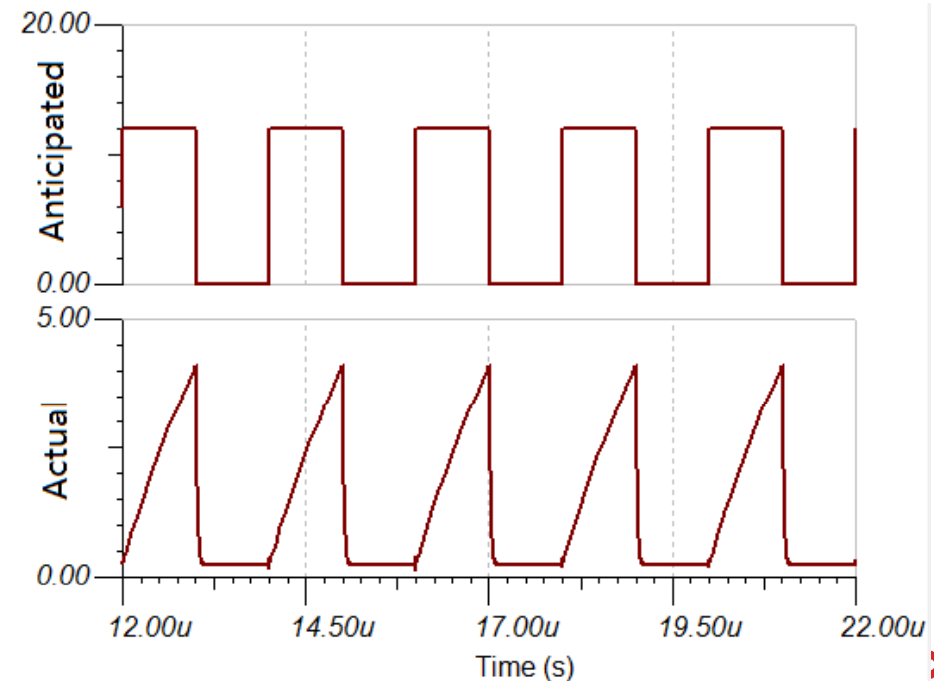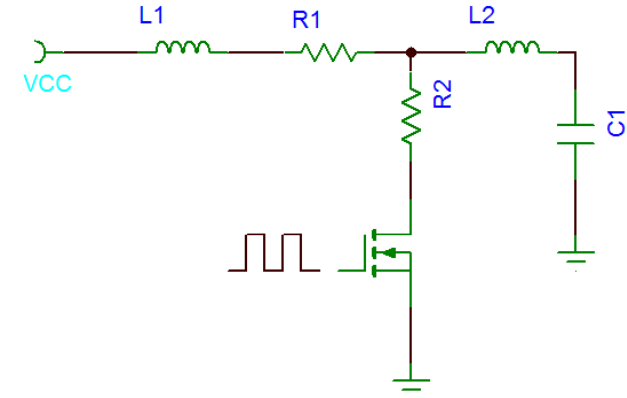

CIRCUIT2

L1=20nH

R1=1ohm

C1=200pF

$$R_2^2 C_1 < 4L_1$$

$$\tau = \frac{2L}{R} = 40ns$$



$$\omega = \sqrt{\frac{4L - R^2 C}{4CL^2}} = 5e8$$

Solution:

Bigger R1?

Narrower trace?

Others?

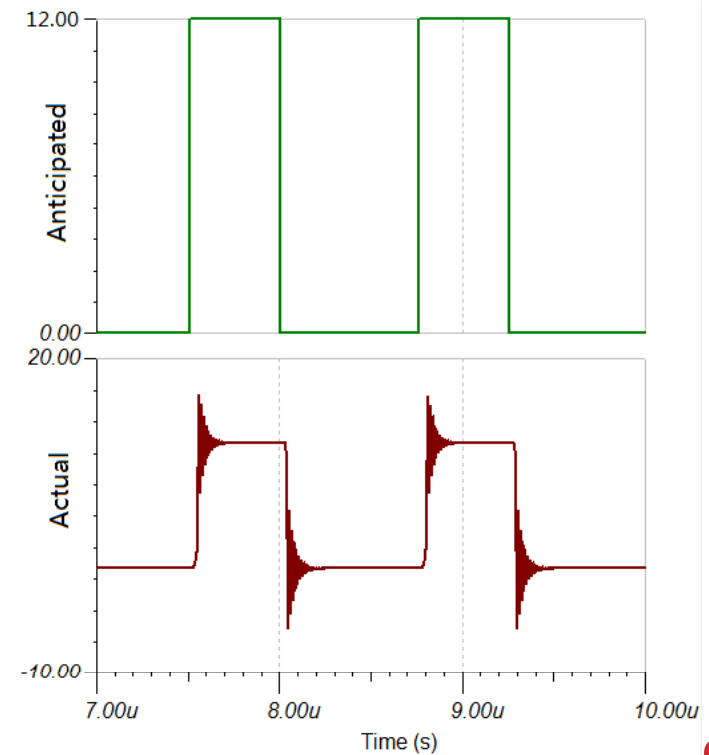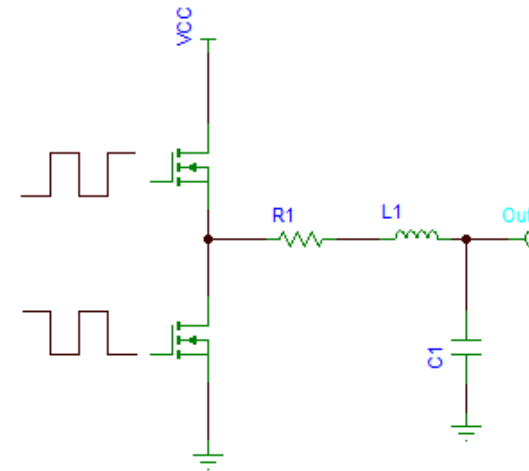

TRANSMISSION LINE

Assume U_{in} is sine wave:

$$U_z = A_1 e^{-jkz} + A_2 e^{jkz}$$

$$I_z = \frac{1}{Z_c} (A_1 e^{-jkz} - A_2 e^{jkz})$$



$$Z_c = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$jk = \sqrt{(R + j\omega L)(G + j\omega C)}$$

If $R \ll \omega L$, $G \ll \omega C$:

$$Z_c = \sqrt{L/C}$$

$$k = \beta = \omega \sqrt{LC}$$

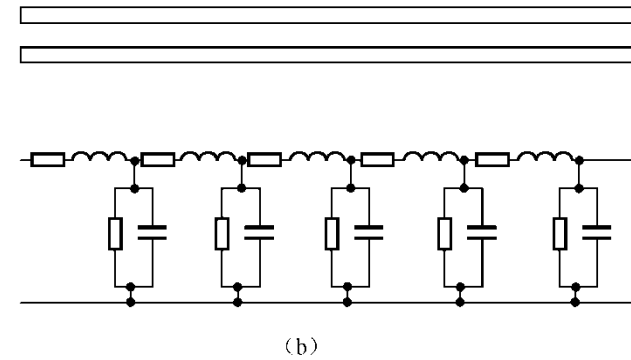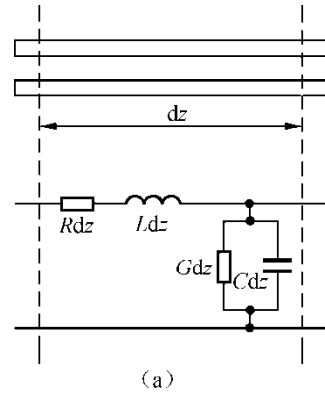


TRACE CHARACTERISTIC IMPEDANCE

T=35.34um (10Z)

ER=4.6 (FR-4)

$$Z_c = \sqrt{L/C}$$

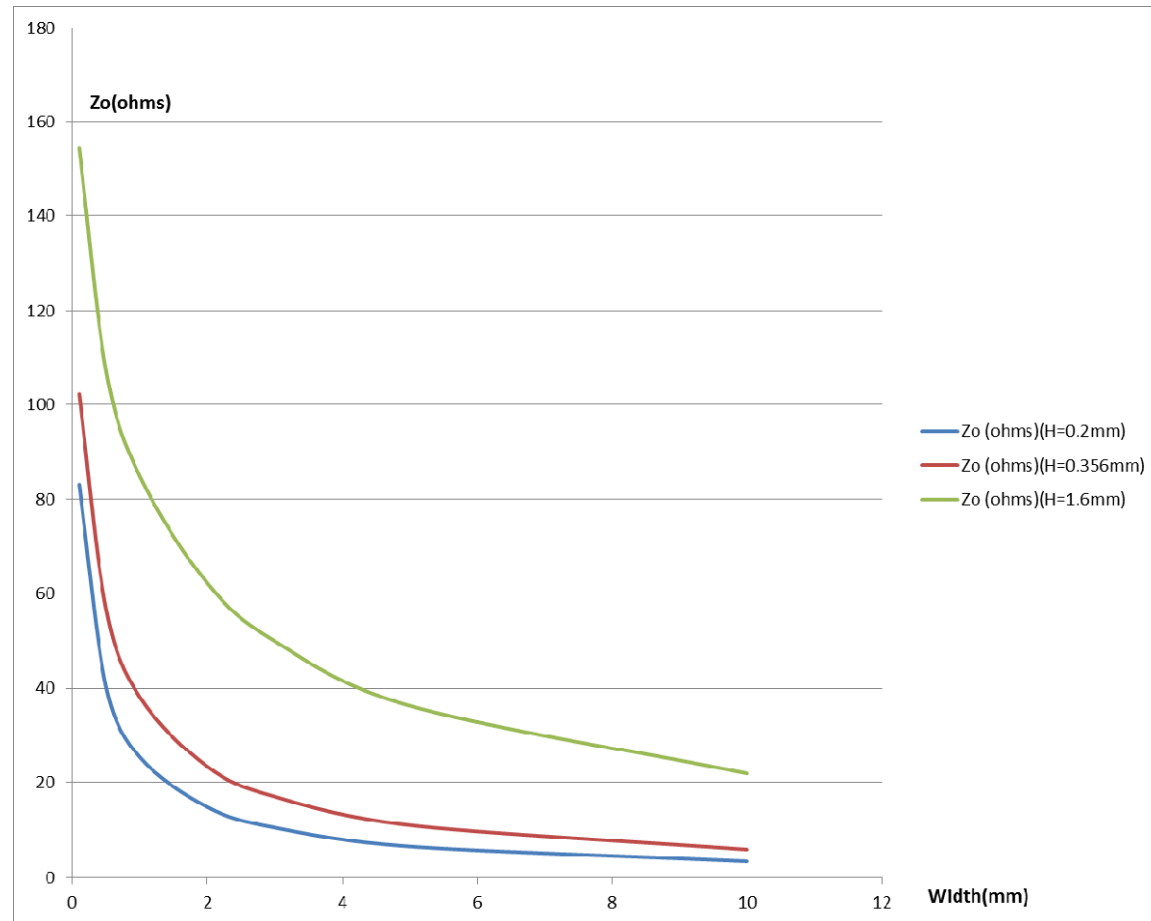

IMPEDANCE MATCHING

$$U(l) = \frac{2U_{in}}{\left(\frac{Z_L + Z_C}{Z_L}\right)e^{j\beta l} + \left(\frac{Z_L - Z_C}{Z_L}\right)e^{-j\beta l}} = \frac{U_{in}}{\left(\frac{\cos(\beta l)}{\cos(h)}\right)e^{jh}}$$

$$h = \arctg\left(\frac{Z_C \tan(\beta l)}{Z_L}\right)$$

$$\beta = \omega \sqrt{LC}$$


reflection coefficient

$$\Gamma = \frac{Z_L - Z_C}{Z_L + Z_C}$$

If $Z_L = Z_C$:

$\Gamma = 0$ (No reflection)

$$U(l) = U_{in} e^{-j\beta l}$$

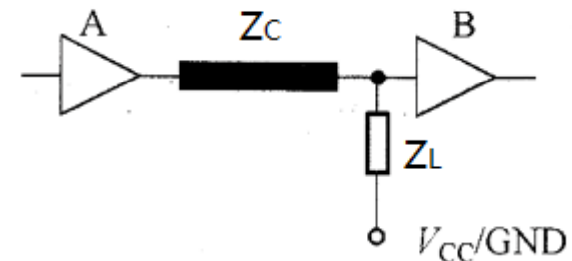


IMPEDANCE MATCHING

$$U(l) = \frac{2U_{in}}{\left(\frac{R_s + Z_c}{Z_c}\right)e^{j\beta l} - \left(\frac{R_s - Z_c}{Z_c}\right)e^{-j\beta l}} = \frac{U_{in}}{\left(\frac{\cos(\beta l)}{\cos(h)}\right)e^{jh}}$$

$$h = \arctg\left(\frac{R_s \tg(\beta l)}{Z_c}\right)$$

$$\beta = \omega \sqrt{LC}$$

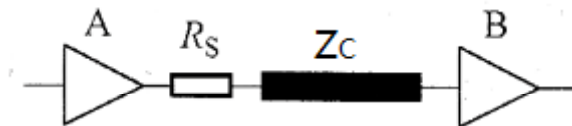



$Z_L = \infty$, $\Gamma = 1$, total reflection.

If $R_s = Z_c$:


$$U(l) = U_{in} e^{-j\beta l}$$

WAVEFORM


$$Z_C = 10, R_S = 50$$

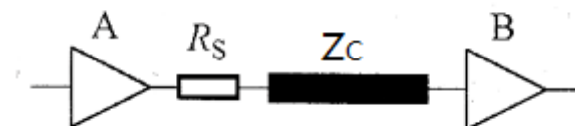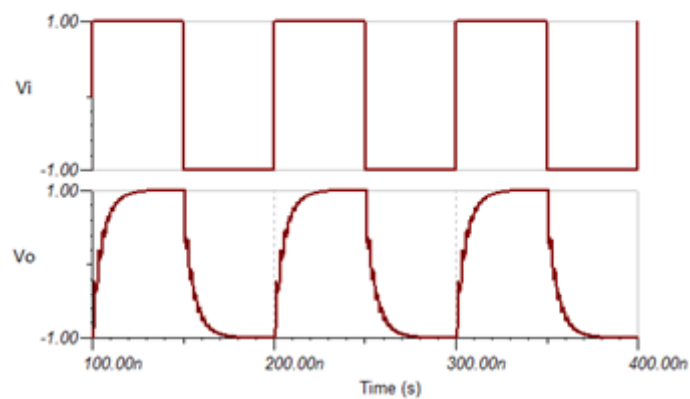

$$Z_C = 10, R_S = 10$$

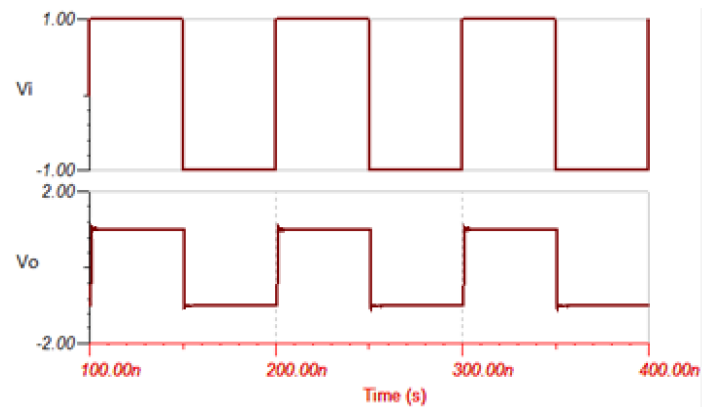

$$Z_C = 10, R_S = 2$$

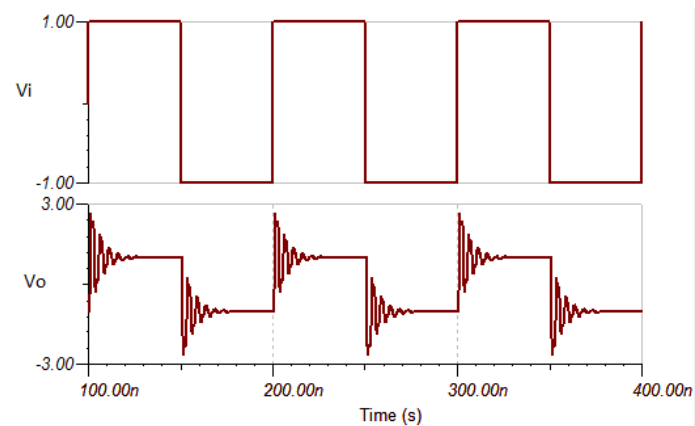

PROPAGATION DELAY TIME

propagation speed $v \approx \frac{c}{\sqrt{\epsilon_r}}$

Propagation delay time $T_{pd} \approx \frac{1 \cdot 10^{10}}{v}$ (ps/cm)

FR4, micro-strip, $T_{pd}=56.4\text{ps/cm}$.

Time shift of two traces is: $t_{err}=\Delta\text{Length} \cdot T_{pd}$

SUMMARY

- Use Saturn to estimate LCR parasitic value.
- Use R , $1/(j\omega C)$, $j\omega L$ to calculate sine signal response.
- For step signal or square signal, use $R^2C - 4L$ to identify properly waveform. Calculate time constant τ .
- If possible, ignore L , C or R to simplify model.
- For high speed or short delay time, use transmission line model. Be aware of impedance matching and length matching.

Thank You